




RBE 2002: Unified Robotics II

Analog Filtering


Prof. Craig Putnam

Filter Types

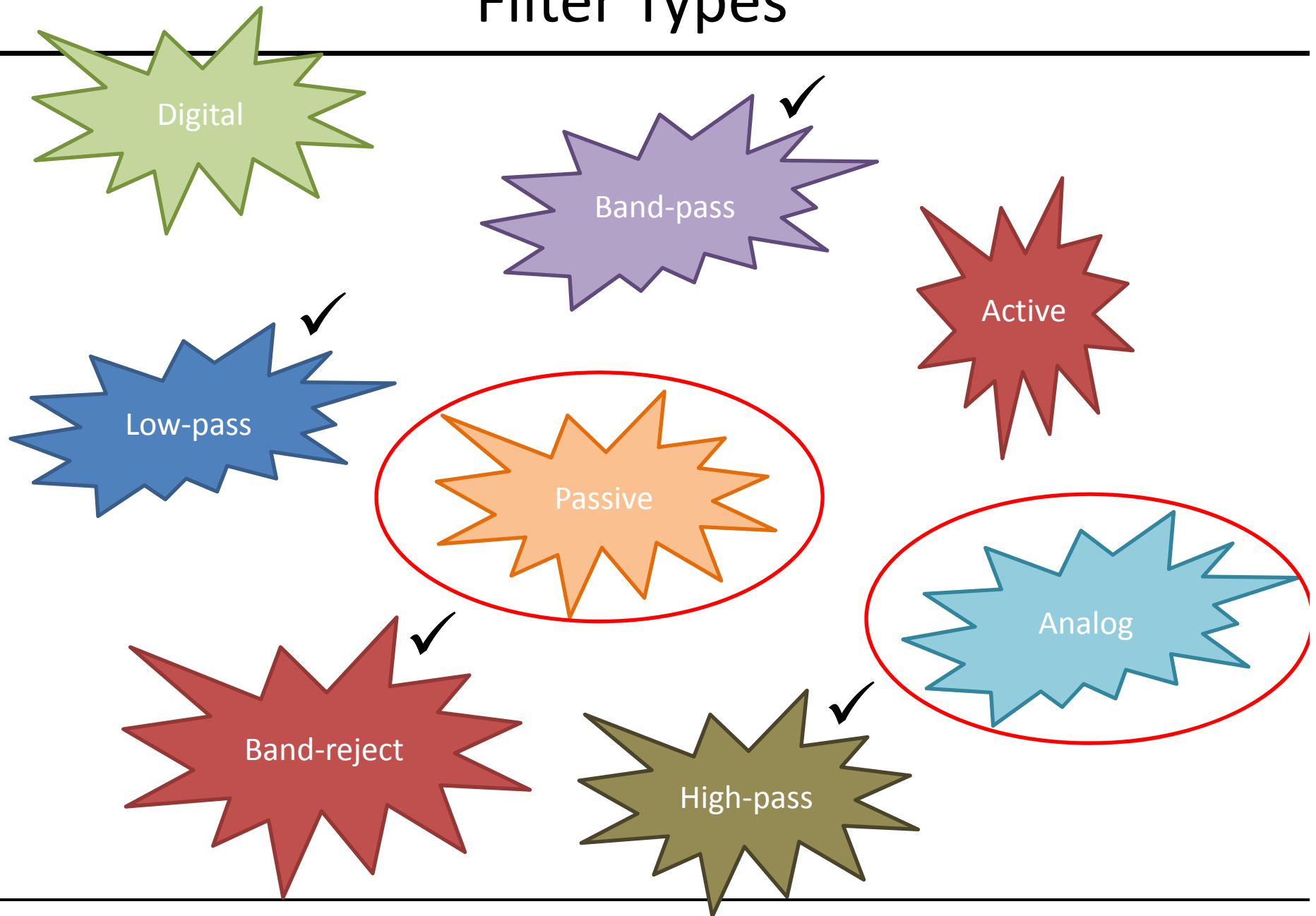


Real World Application

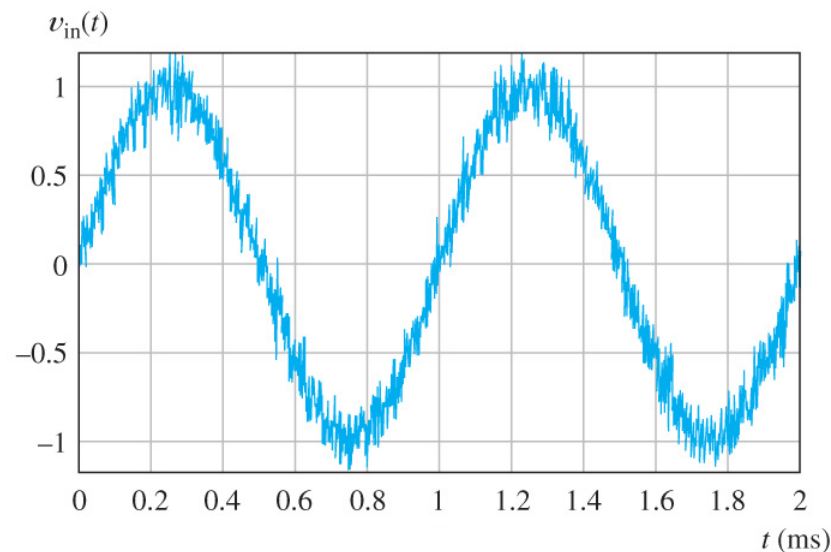- ✓ Suppose you have a sensor on your robot that is generating a sinusoidal signal
- ✓ Also suppose there is some high frequency noise that is being picked up by the sensor & wiring
- ✓ How might you deal with this?



Real World Application

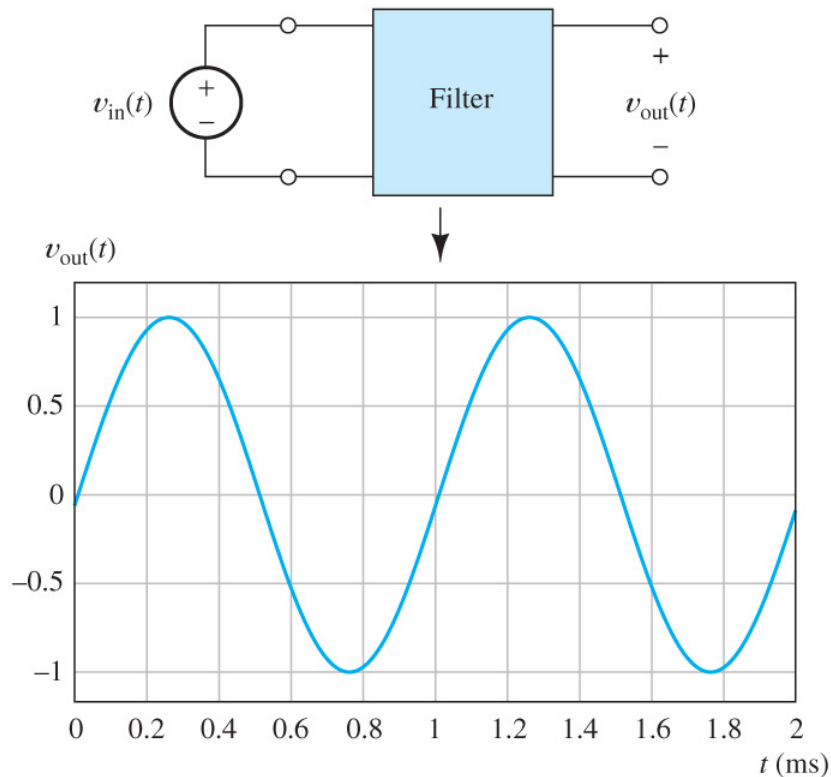- ✓ Send the noisy signal through a low pass filter
- ✓ If the filter is set up properly, the high frequencies are removed and you are left with a clean signal





Ideal Filters

- ✓ An ideal filter passes frequencies in the desired range with no change at all, and completely rejects frequencies outside of that range
- ✓ What kinds of filters might there be?
 - ◆ Low pass
 - ◆ High pass
 - ◆ Band pass
 - ◆ Band reject

Real Filters

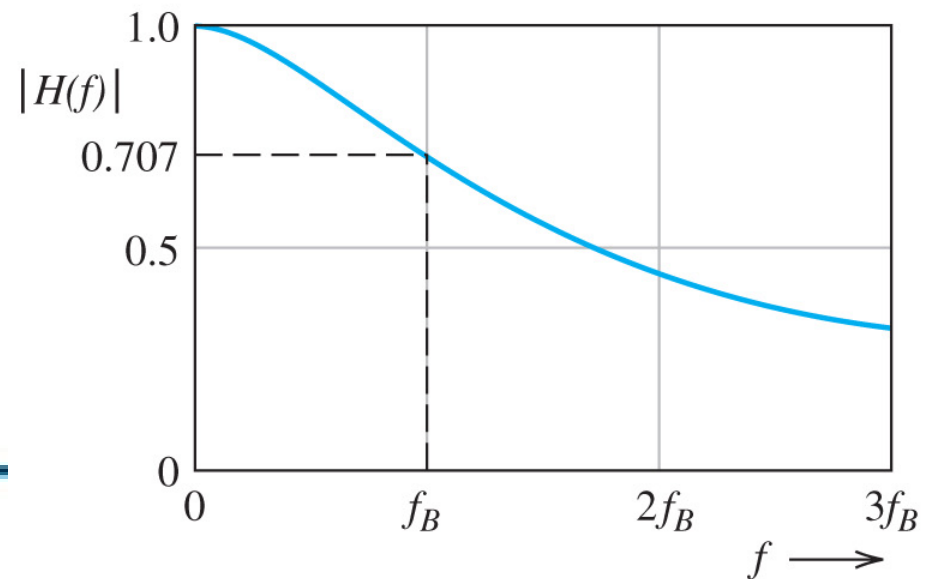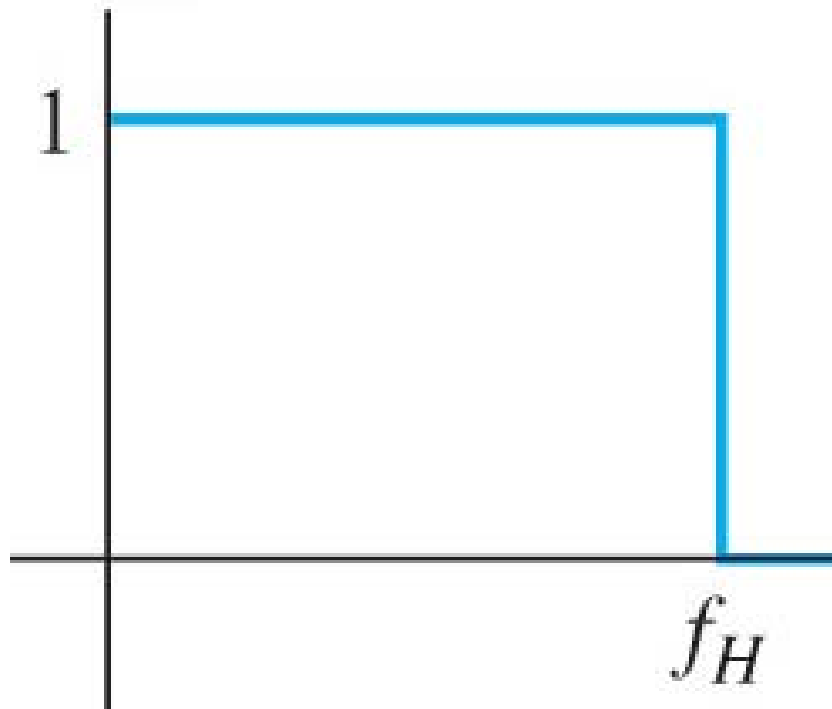- ✓ It is difficult to create real filters that behave in the same way as ideal filters
- ✓ That said, real filters can be (and are) very effective
- ✓ We will concentrate today on passive, analog filters



Frequency Characteristics

- ✓ We will construct our passive, analog filters out of the following components:
 - ◆ Resistors
 - ◆ Capacitors
 - ◆ Inductors
- ✓ First we will need to examine the frequency characteristics of these devices
- ✓ We also need to define the term *impedance*

$$\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}}$$


Impedance Characteristics

✓ Resistors $\frac{\mathbf{V}}{\mathbf{I}} = R$


✓ Capacitors $\frac{\mathbf{V}}{\mathbf{I}} = \frac{1}{j\omega C} = \frac{1}{j2\pi fC} = -j \frac{1}{2\pi fC}$

✓ Inductors $\frac{\mathbf{V}}{\mathbf{I}} = j\omega L = j2\pi fL$

Impedance Characteristics

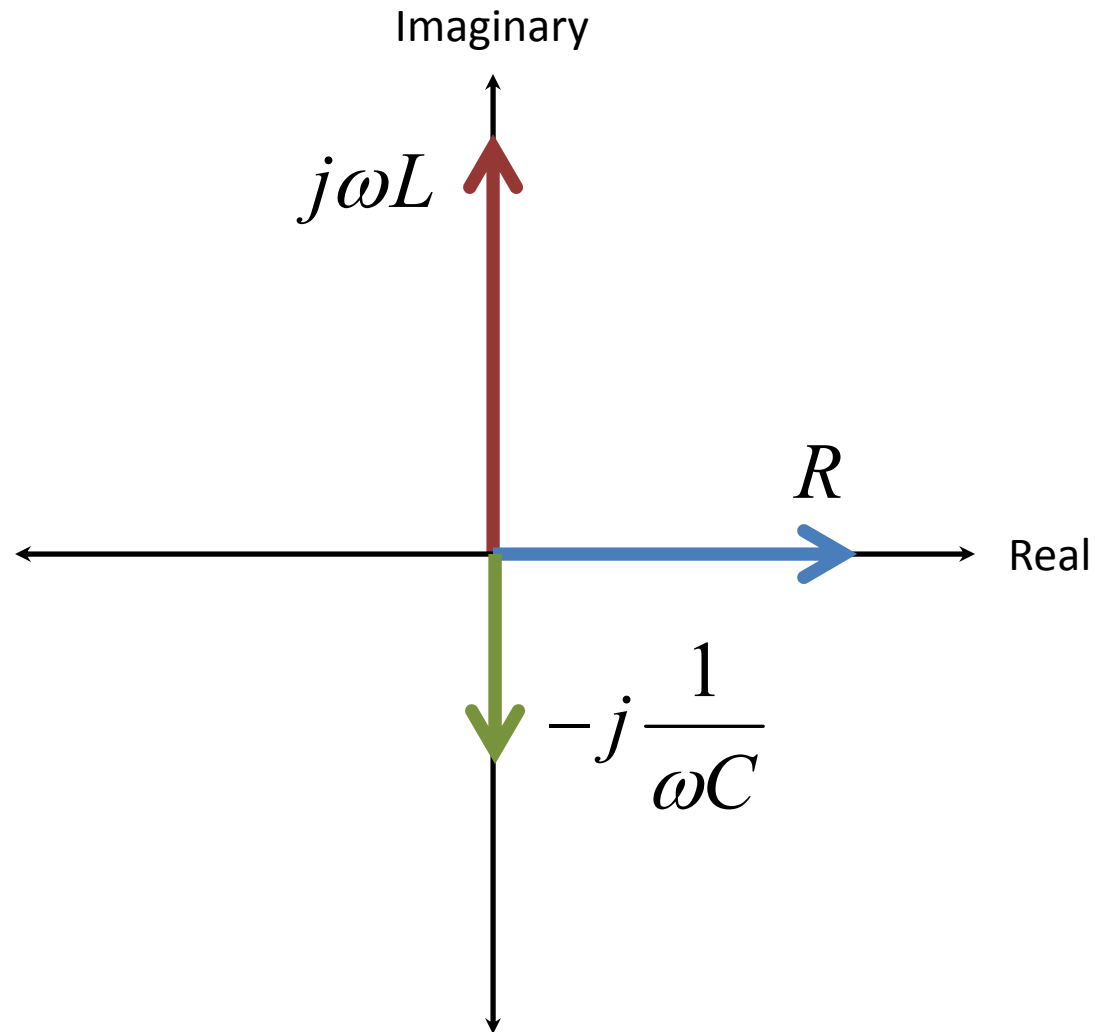

Impedance Characteristics

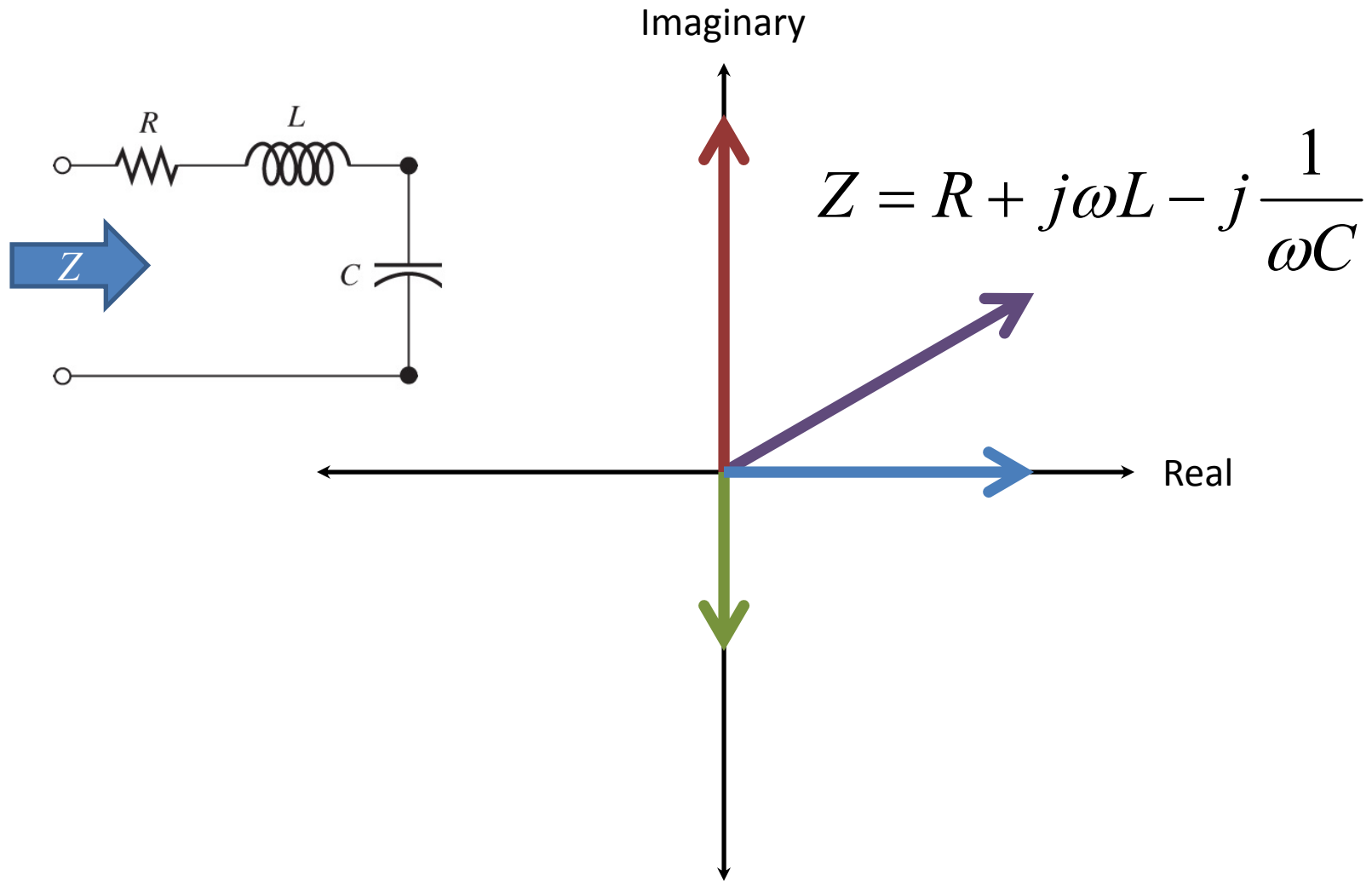

Frequency Characteristics

✓ Capacitors $\frac{\mathbf{V}}{\mathbf{I}} = \frac{1}{j\omega C} = \frac{1}{j2\pi fC}$

♦ At low frequencies: $\lim_{f \rightarrow 0} \frac{1}{j2\pi fC} \rightarrow \infty$

♦ At high frequencies: $\lim_{f \rightarrow \infty} \frac{1}{j2\pi fC} \rightarrow 0$

Frequency Characteristics


✓ Inductors $\frac{\mathbf{V}}{\mathbf{I}} = j\omega L = j2\pi fL$

♦ At low frequencies: $\lim_{f \rightarrow 0} j2\pi fl \rightarrow 0$

♦ At high frequencies: $\lim_{f \rightarrow \infty} j2\pi fl \rightarrow \infty$

Introduction to Phasors

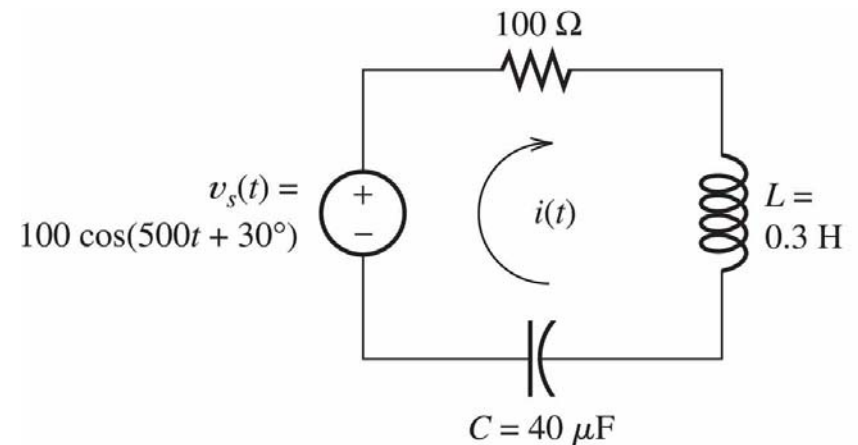- ✓ Imagine a circuit with a steady-state sinusoidal excitation



- ✓ In the general case, we can write this as:

$$v(t) = A \cos(\omega t + \phi)$$

Introduction to Phasors

- ✓ Actually, let's suppose that things are in reality more complicated – that the excitation signal is as follows:

$$v(t) = 10 \cos(\omega t) + 5 \sin(\omega t + 60^\circ) + 5 \cos(\omega t + 90^\circ)$$

- ✓ You could use trig identities and with a fair amount of work get to an answer
- ✓ But there is an easier way to approach the problem

Introduction to Phasors

- ✓ For a sinusoidal voltage of the form:

$$v_1(t) = A_1 \cos(\omega t + \phi_1)$$

we define the phasor as:

$$\mathbf{V}_1 = V_1 \cos \angle \phi_1$$

- ✓ A phasor for a sinusoid is therefore a complex number having a magnitude equal to the peak value and having a phase angle the same as the sinusoid

Introduction to Phasors

- ✓ Suppose we have a sinusoidal voltage of the form:

$$v_2(t) = A_2 \sin(\omega t + \phi_2)$$

- ✓ In this case we first convert it back to a cosine function using the trig identity:

$$\sin(z) = \cos(z - 90^\circ)$$

- ✓ This gives us:

$$v_2(t) = A_2 \cos(\omega t + \phi_2 - 90^\circ)$$

$$\mathbf{V}_2 = V_2 \cos \angle(\phi_2 - 90^\circ)$$

Introduction to Phasors

- ✓ We are now in a position to deal with our original complicated case:

$$v(t) = 10 \cos(\omega t) + 5 \sin(\omega t + 60^\circ) + 5 \cos(\omega t + 90^\circ)$$

- ✓ We begin by converting everything back to cosine functions:

$$v(t) = 10 \cos(\omega t) + 5 \cos(\omega t - 30^\circ) + 5 \cos(\omega t + 90^\circ)$$

Introduction to Phasors

✓ Recall Euler's identity:

$$\cos(\theta) = \operatorname{Re}(e^{j\theta}) = \operatorname{Re}[\cos(\theta) + j\sin(\theta)]$$

✓ We can write our original equation:

$$v(t) = 10\cos(\omega t) + 5\cos(\omega t - 30^\circ) + 5\cos(\omega t + 90^\circ)$$

as:

$$v(t) = 10\operatorname{Re}[e^{j\omega t}] + 5\operatorname{Re}[e^{j(\omega t - 30^\circ)}] + 5\operatorname{Re}[e^{j(\omega t + 90^\circ)}]$$

Introduction to Phasors

✓ We can bring the scalar inside, resulting in:

$$v(t) = \operatorname{Re}\left[10e^{j\omega t}\right] + \operatorname{Re}\left[5e^{j(\omega t - 30^\circ)}\right] + \operatorname{Re}\left[5e^{j(\omega t + 90^\circ)}\right]$$

and then group the terms as:

$$v(t) = \operatorname{Re}\left[10e^{j\omega t} + 5e^{j(\omega t - 30^\circ)} + 5e^{j(\omega t + 90^\circ)}\right]$$

✓ We now can factor out the common term $e^{j\omega t}$ to get:

$$v(t) = \operatorname{Re}\left[\left(10 + 5e^{-j30^\circ} + 5e^{j90^\circ}\right)e^{j\omega t}\right]$$

Introduction to Phasors

- ✓ The complex numbers can now be put in polar form:

$$v(t) = \text{Re} \left[\left(10 \angle (0^\circ) + 5 \angle (-30^\circ) + 5 \angle (90^\circ) \right) e^{j\omega t} \right]$$

- ✓ We now combine the complex numbers:

$$\begin{aligned} 10 \angle (0^\circ) + 5 \angle (-30^\circ) + 5 \angle (90^\circ) &= 10 + 4.33 - j2.5 + j5 \\ &= 14.33 + j2.5 \\ &= 14.54 \angle 9.90^\circ \\ &= 14.54 e^{j9.90^\circ} \end{aligned}$$

Introduction to Phasors

✓ The result is:

$$\begin{aligned}v(t) &= \operatorname{Re} \left[\left(14.54 e^{j9.90^\circ} \right) e^{j\omega t} \right] \\&= \operatorname{Re} \left[14.54 e^{j(\omega t + 9.90^\circ)} \right] \\&= 14.54 \cos(\omega t + 9.90^\circ)\end{aligned}$$

Whew!!!

That actually wasn't
all that easy...

Introduction to Phasors

✓ Let's try this once again, but this time we'll take a shortcut...

✓ Here is our original signal:

$$v(t) = 10 \cos(\omega t) + 5 \sin(\omega t + 60^\circ) + 5 \cos(\omega t + 90^\circ)$$

✓ The shortcut is to simply write them as phasors using this notation:

$$\mathbf{V}_x = V_x \angle \phi_x$$

Introduction to Phasors

✓ The gives us:

$$v(t) = 10 \cos(\omega t) + 5 \sin(\omega t + 60^\circ) + 5 \cos(\omega t + 90^\circ)$$



$$\mathbf{V}_1 = V_1 \cos \angle \phi_1 = 10 \angle (0^\circ)$$

$$\mathbf{V}_2 = V_2 \cos \angle \phi_2 = 5 \angle (-30^\circ)$$

$$\mathbf{V}_3 = V_3 \cos \angle \phi_3 = 5 \angle (90^\circ)$$

Introduction to Phasors

✓ We can now add the phasors as before:


$$\begin{aligned}\mathbf{V} &= \mathbf{V}_1 + \mathbf{V}_2 + \mathbf{V}_3 \\ &= 10\angle(0^\circ) + 5\angle(-30^\circ) + 5\angle(90^\circ) \\ &= 10 + 4.33 - j2.5 + j5 \\ &= 14.33 + j2.5 \\ &= 14.54\angle(9.90^\circ)\end{aligned}$$

✓ Converting back to the time domain, we get:

$$v(t) = 14.54 \cos(\omega t + 9.90^\circ)$$

Introduction to Phasors

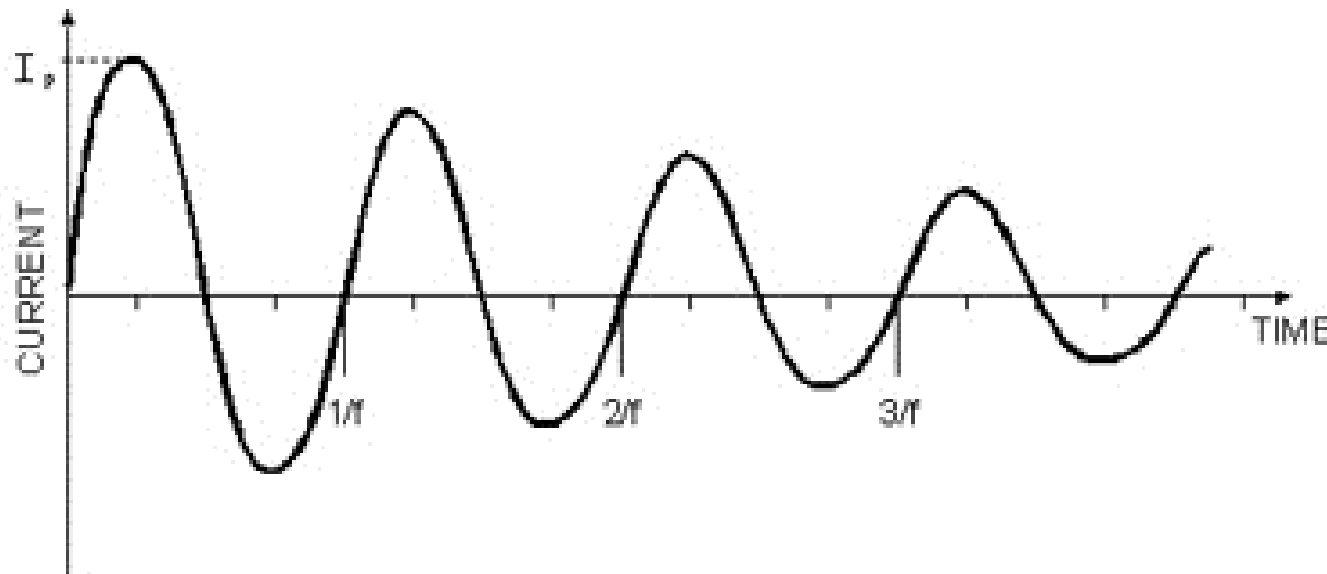- ✓ We said this was true for the case of steady-state sinusoidal excitation
- ✓ Let's now extend this to another interesting class of waveforms, the damped sinusoid



Introduction to Phasors

- ✓ The most general form of a damped sinusoid is:

$$v(t) = Ae^{\sigma t} \cos(\omega t + \phi)$$

where the constant σ is real and (usually) negative or zero

- ✓ If σ is zero, this corresponds to an undamped sinusoid
- ✓ We can easily extend our existing definitions of phasor voltages and currents to account for damped sinusoids if we make just a slight change...

Introduction to Phasors

- ✓ We define a new variable s which we will call...
- ✓ ...the complex frequency
- ✓ We define it as:

$$s = \sigma + j\omega$$

- ✓ Let's look at the special case where $\sigma = 0$

$$s = j\omega$$

Introduction to Phasors

- ✓ We can start with a time-domain representation of a circuit's behavior:

$$v(t) = A \cos(\omega t + \phi)$$

- ✓ This in turn can be represented using phasor notation:

$$\mathbf{V}(j\omega) = Ae^{j\phi} = A\angle\phi$$

- ✓ Then with another simple change of variable we end up with:

$$\mathbf{V}(s) = Ae^{j\phi} = A\angle\phi$$

- ✓ From this we see that phasor analysis is equivalent to using the Laplace Transform

Laplace Transform

✓ Resistors $Z_R(s) = \frac{\mathbf{V}(s)}{\mathbf{I}(s)} = R$

✓ Capacitors $Z_C(s) = \frac{\mathbf{V}(s)}{\mathbf{I}(s)} = \frac{1}{j\omega C} = \frac{1}{sC}$

✓ Inductors $Z_L(s) = \frac{\mathbf{V}(s)}{\mathbf{I}(s)} = j\omega L = sL$

Example: Laplace Transform

✓ Lets determine the frequency response of a series RL circuit using the Laplace Transform


✓ Assume:

$$v_s(t) = 10e^{-2t} \cos(5t) \text{ V}$$

where

$$R = 4\Omega; L = 2H$$

✓ Therefore: $s = -2 + 5j$

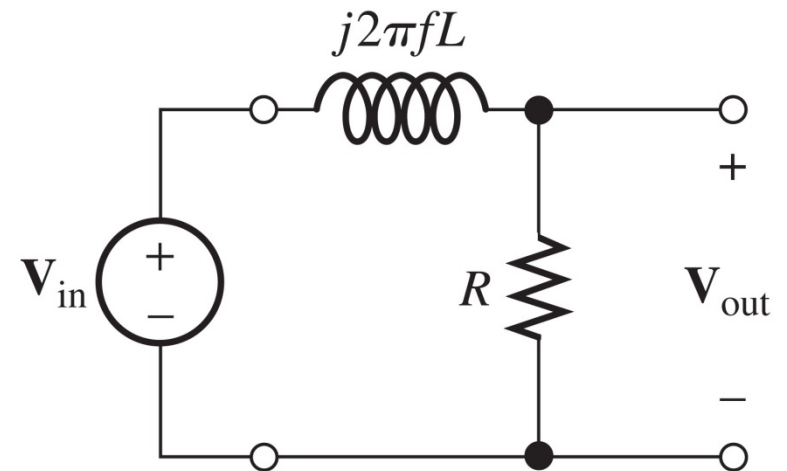

Copyright © 2008 Pearson Prentice Hall, Inc.


Example: Laplace Transform

- ✓ The input phasor is given by:

$$\mathbf{V}(s) = 10\angle 0^\circ \text{V}$$

- ✓ The impedance seen by the voltage source is:


$$Z(s) = R + sL = 4 + 2s$$

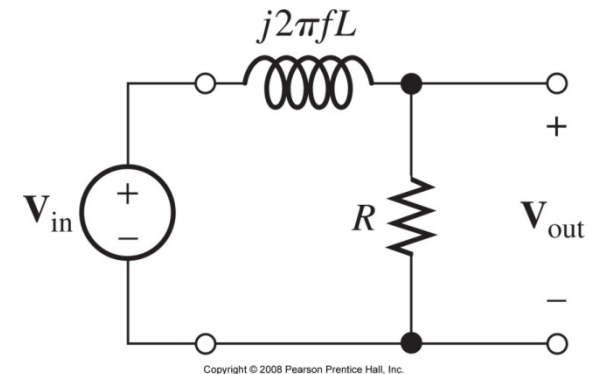

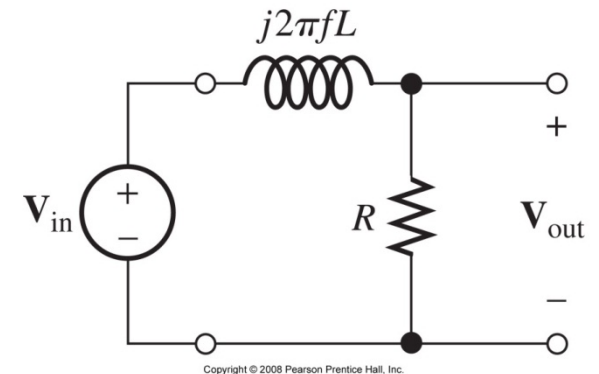Example: Laplace Transform

✓ The series current is therefore:


$$\begin{aligned}\mathbf{I}(s) &= \frac{\mathbf{V}(s)}{Z(s)} = \frac{10}{4 + 2s} = \frac{10}{4 + 2(-2 + j5)} \\ &= \frac{10}{j10} = j1 = 1 \angle \left(-\frac{\pi}{2} \right)\end{aligned}$$



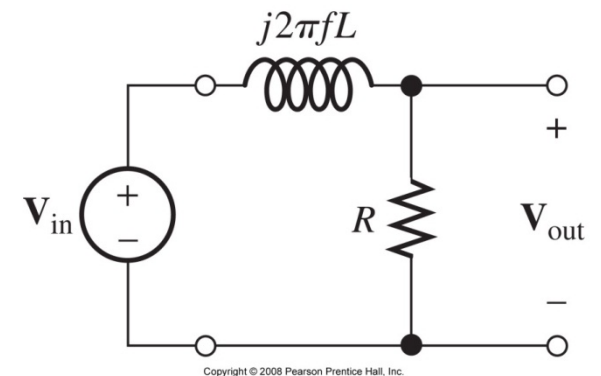Example: Laplace Transform


- ✓ Finally, the time-domain expression for the current is given by:

$$i_s(t) = e^{-2t} \cos\left(5t - \frac{\pi}{2}\right) \text{ A}$$




Low-Pass Filters

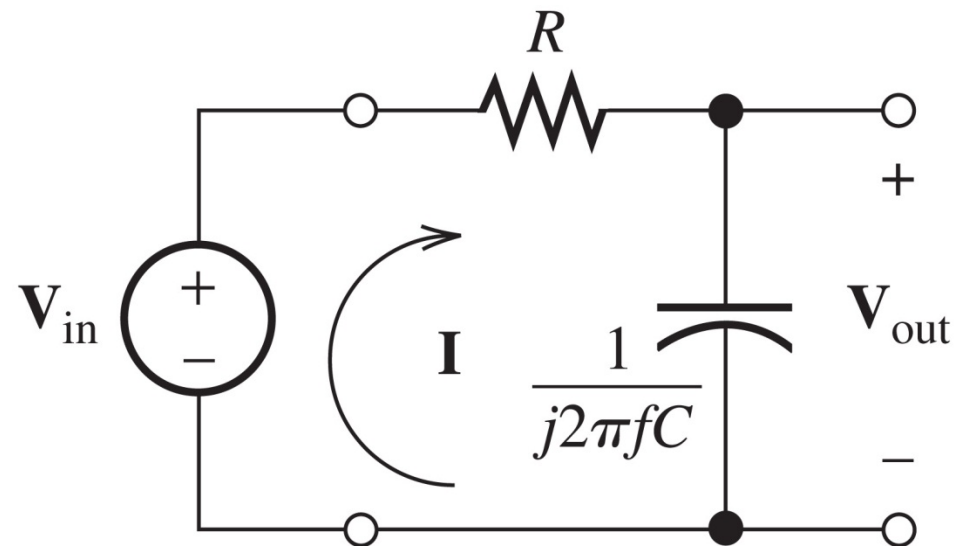- ✓ Now that we have the background behind us, lets design a low-pass filter
- ✓ As the name implies, we want to pass the low frequencies
- ✓ The circuit shown at the right will do this




Copyright © 2008 Pearson Prentice Hall, Inc.

First Order RC Low-Pass Filter

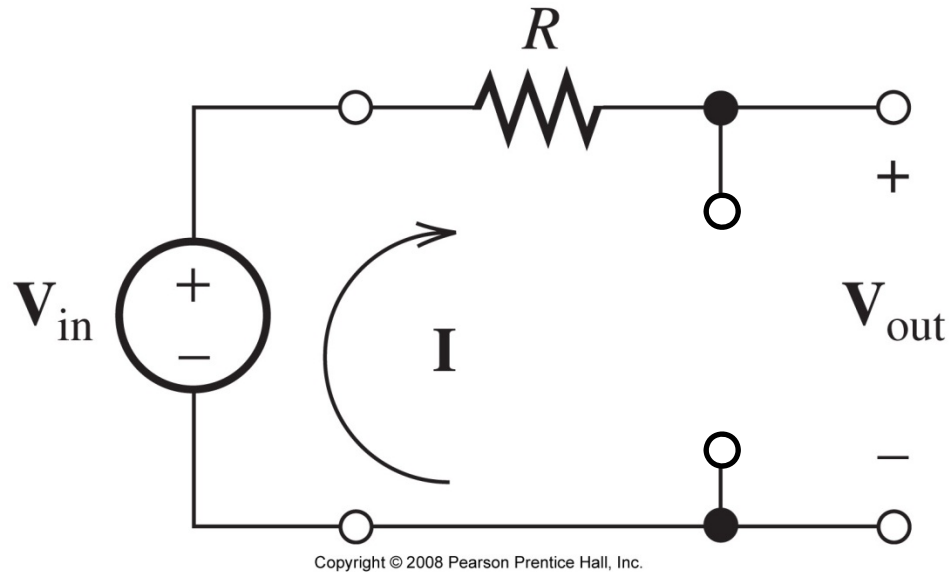


- ✓ At low frequencies, the capacitor has high impedance
- ✓ It therefore acts like an open circuit
- ✓ $V_{out} \approx V_{in}$

First Order RC Low-Pass Filter

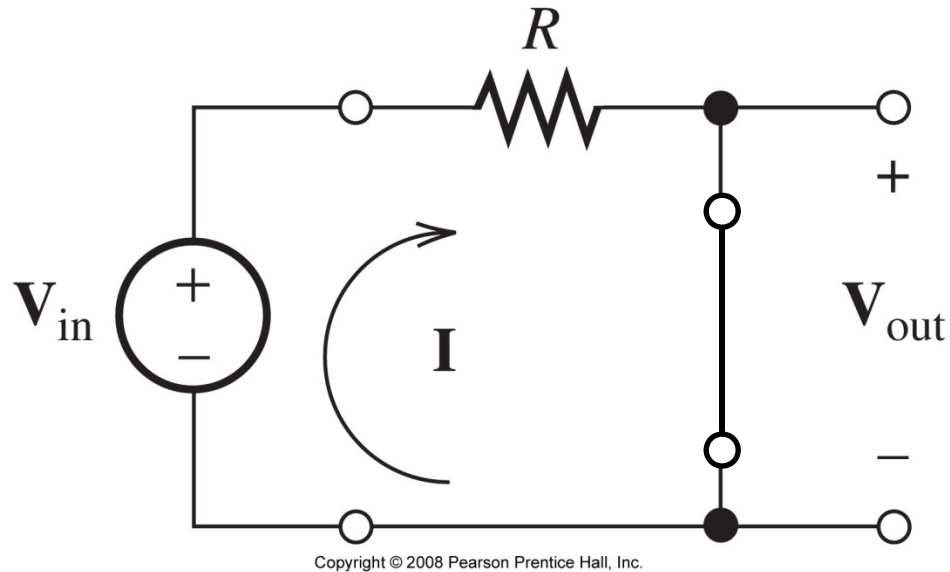

- ✓ At high frequencies, the capacitor has low impedance
- ✓ It therefore acts like an short circuit
- ✓ $V_{\text{out}} \approx 0$

First Order RC Low-Pass Filter

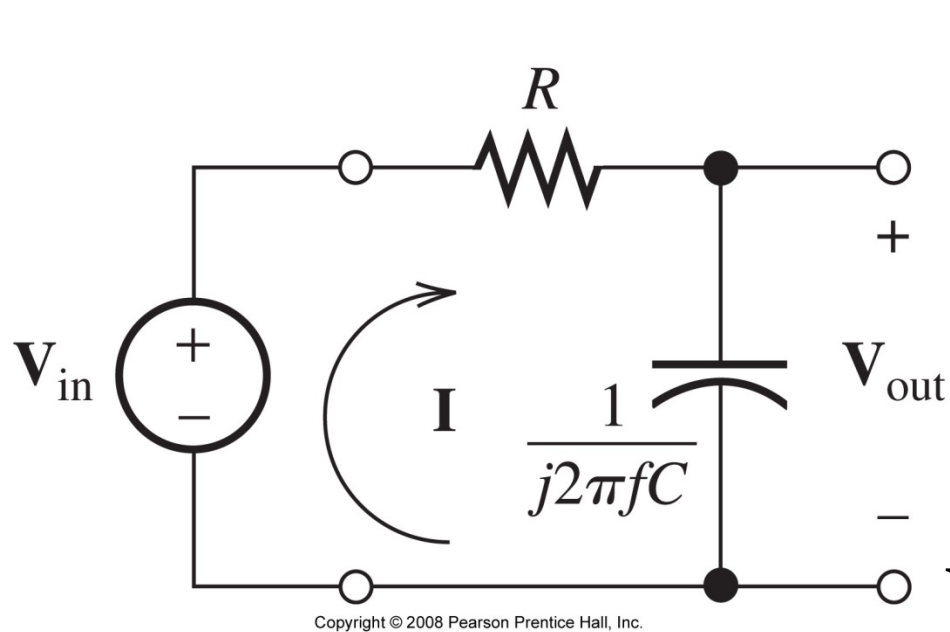


$$\mathbf{I} = \frac{\mathbf{V}_{\text{in}}}{R + 1/j2\pi fC}$$

$$\mathbf{V}_{\text{out}} = \frac{1}{j2\pi fC} \mathbf{I}$$

$$\mathbf{V}_{\text{out}} = \frac{1}{j2\pi fC} \times \frac{\mathbf{V}_{\text{in}}}{R + 1/j2\pi fC}$$

$$H(f) = \frac{\mathbf{V}_{\text{out}}}{\mathbf{V}_{\text{in}}} = \frac{1}{1 + j2\pi fRC}$$

First Order RC Low-Pass Filter

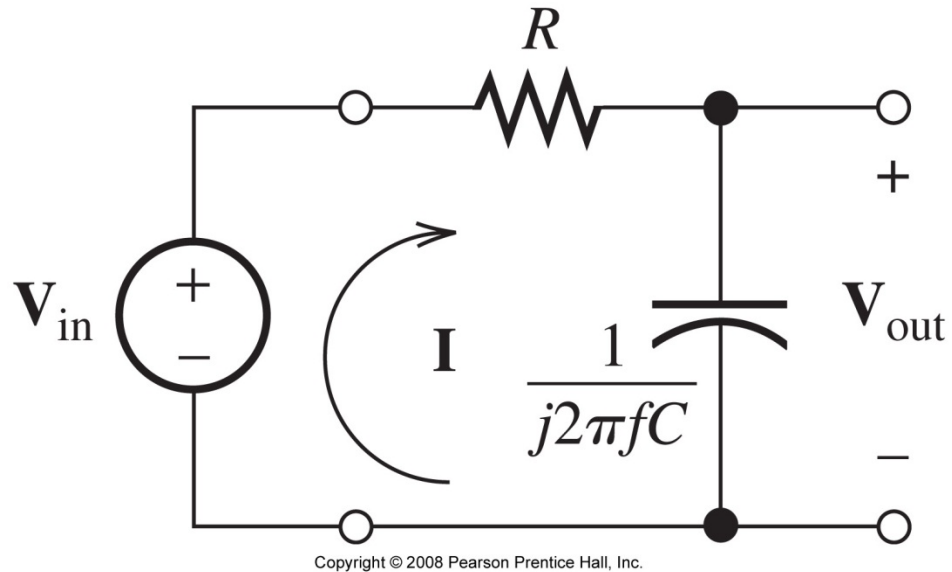


$$H(f) = \frac{\mathbf{V}_{\text{out}}}{\mathbf{V}_{\text{in}}} = \frac{1}{1 + j2\pi fRC}$$

$$f_B = \frac{1}{2\pi RC}$$

$$H(f) = \frac{1}{1 + j(f/f_B)}$$



First Order RC Low-Pass Filter

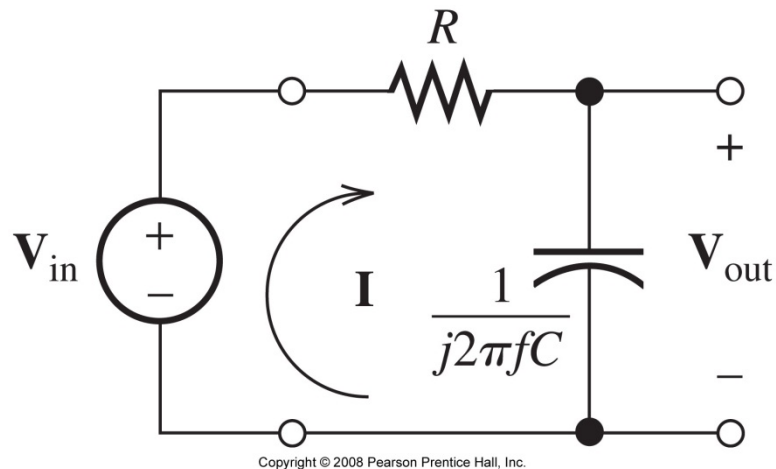


$$H(f) = \frac{1}{1 + j(f/f_B)}$$

$$|H(f)| = \frac{1}{\sqrt{1 + (f/f_B)^2}}$$

$$\angle H(f) = -\arctan(f/f_B)$$

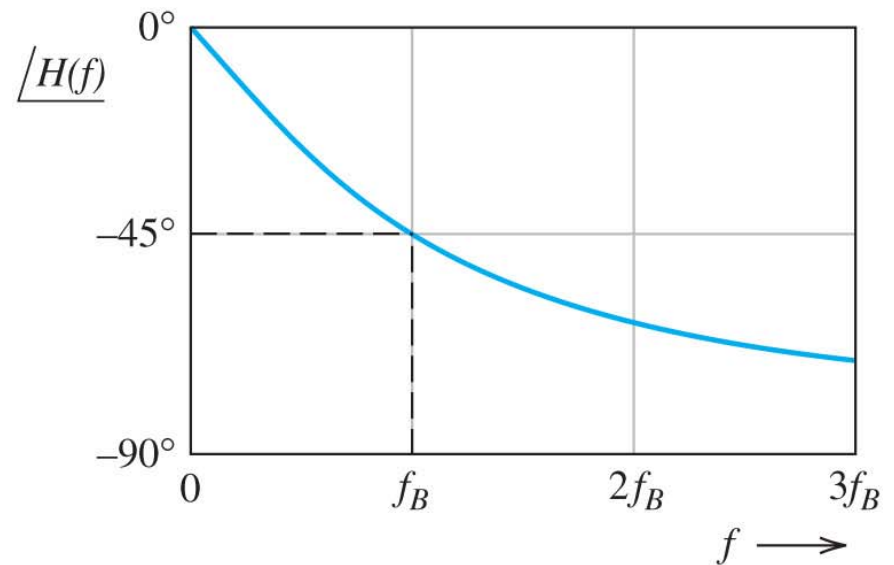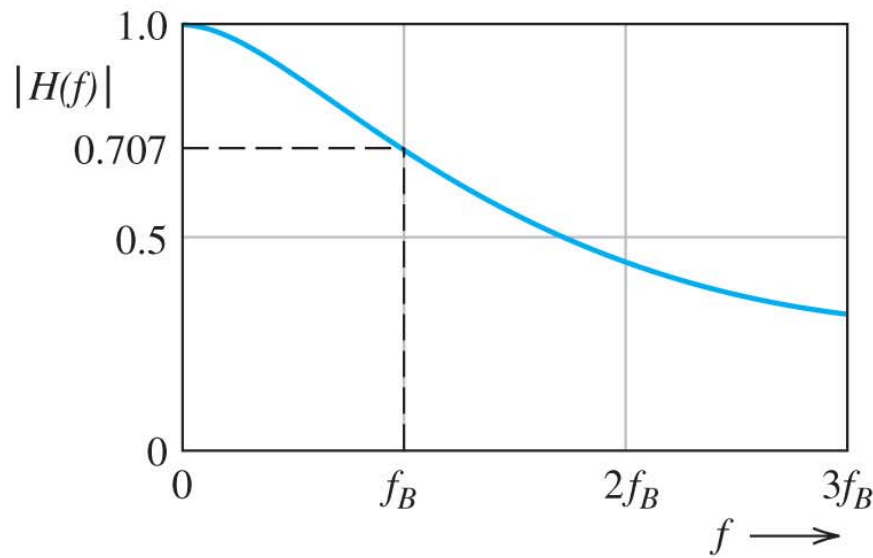

Example of RC Low Pass Filter

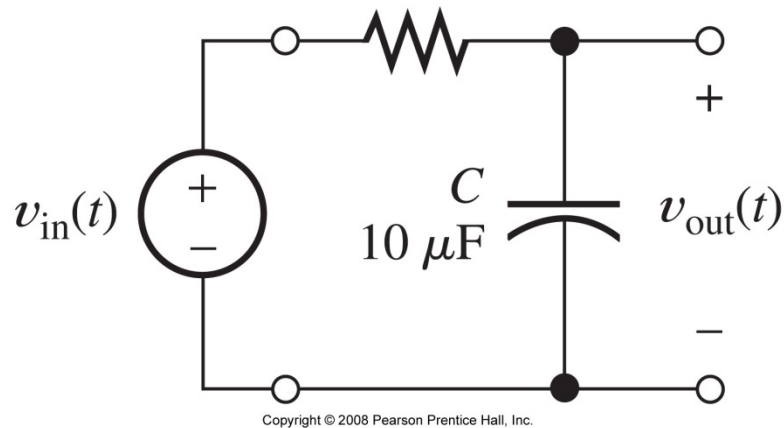


✓ We want $f_B = 100$ Hz

$$f_B = \frac{1}{2\pi RC} = 100 \text{ Hz}$$
$$= \frac{1}{2\pi R \times (10 \times 10^{-6})}$$

$$R = \frac{1000}{2\pi} = 159.2\Omega$$

Example of RC Low Pass Filter

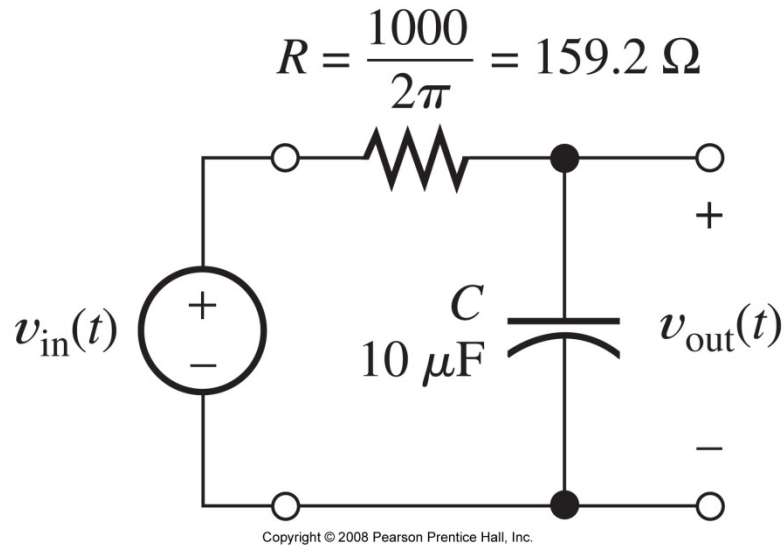


✓ Suppose the input voltage is as follows:

$$v_{in}(t) = 5 \cos(20\pi t) \\ + 5 \cos(200\pi t) \\ + 5 \cos(2000\pi t)$$

✓ Let $v_{in1}(t) = 5 \cos(20\pi t)$

✓ Using phasor notation, this is $\mathbf{V}_{in1} = 5 \angle 0^\circ$
with an angular frequency of $\omega = 20\pi$; $f = \frac{\omega}{2\pi} = 10 \, \text{Hz}$

Example of RC Low Pass Filter

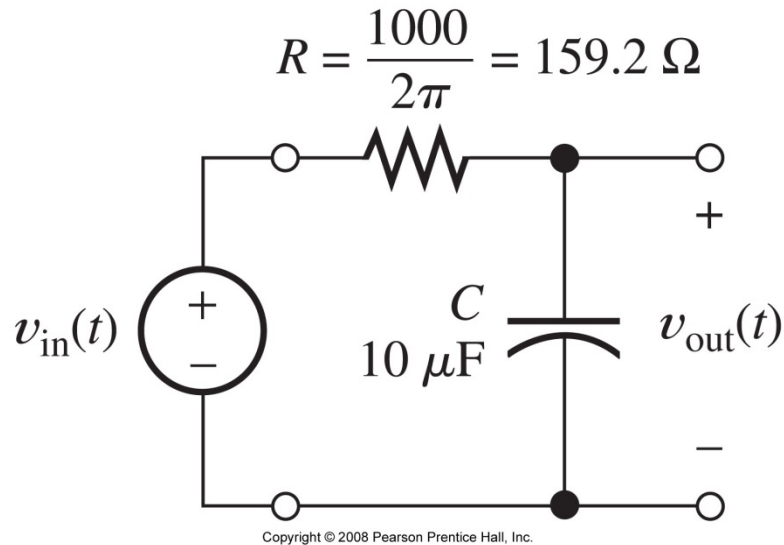


✓ We now apply the transfer function at f_1 :

$$H(f_1) = \frac{1}{1 + j(f_1/f_B)}$$

$$\begin{aligned} H(10) &= \frac{1}{1 + j(10/100)} \\ &= 0.9950 \angle -5.71^\circ \end{aligned}$$

$$\begin{aligned} \mathbf{V}_{\text{out}1} &= H(10) \times \mathbf{V}_{\text{in}1} \\ &= (0.9950 \angle -5.71^\circ) \times (5 \angle 0^\circ) = 4.975 \angle -5.71^\circ \end{aligned}$$

Example of RC Low Pass Filter

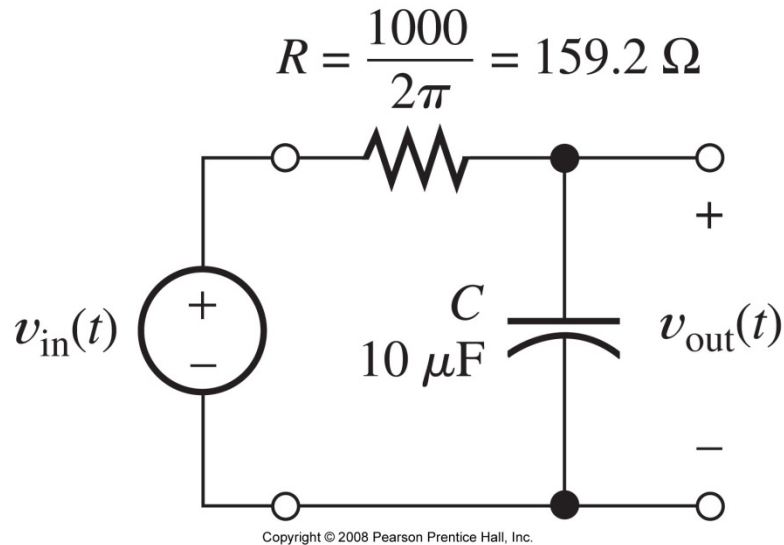


✓ Repeating the process for the 2nd and 3rd components of \mathbf{V}_{in} at frequencies f_2 and f_3 we get the following:

$$\begin{aligned}\mathbf{V}_{out2} &= H(100) \times \mathbf{V}_{in2} \\ &= (0.7071 \angle -45^\circ) \times (5 \angle 0^\circ) = 3.535 \angle -45^\circ\end{aligned}$$

$$\begin{aligned}\mathbf{V}_{out3} &= H(1000) \times \mathbf{V}_{in3} \\ &= (0.0995 \angle -84.29^\circ) \times (5 \angle 0^\circ) = 0.4975 \angle -84.29^\circ\end{aligned}$$

Example of RC Low Pass Filter

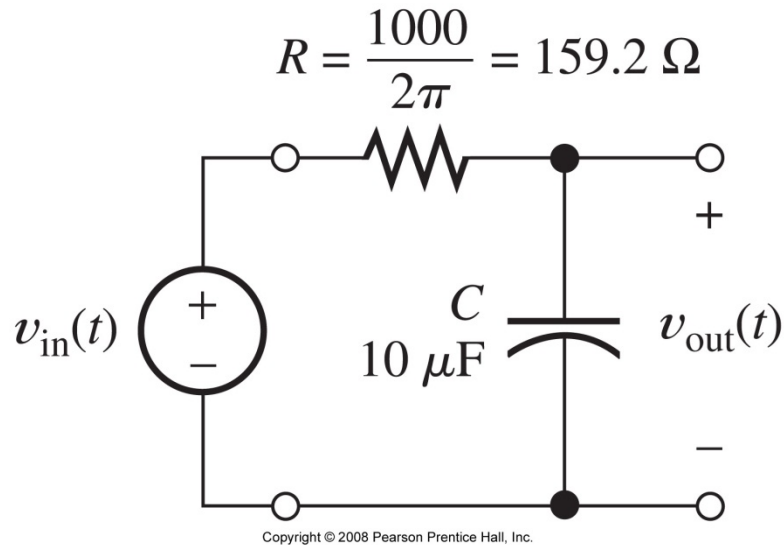


✓ Adding all of the components together gives us:

$$\begin{aligned}\mathbf{V}_{\text{out}} &= \mathbf{V}_{\text{out1}} + \mathbf{V}_{\text{out2}} + \mathbf{V}_{\text{out3}} \\ &= \left(4.975 \angle -5.71^\circ\right) \\ &\quad + \left(3.535 \angle -45^\circ\right) \\ &\quad + \left(0.4975 \angle -84.29^\circ\right)\end{aligned}$$

$$\begin{aligned}\mathbf{V}_{\text{out}} &= 4.975 \cos\left(20\pi t - 5.71^\circ\right) + 3.535 \cos\left(200\pi t - 45^\circ\right) \\ &\quad + 0.4975 \cos\left(2000\pi t - 84.29^\circ\right)\end{aligned}$$

Alternative Low Pass Filter

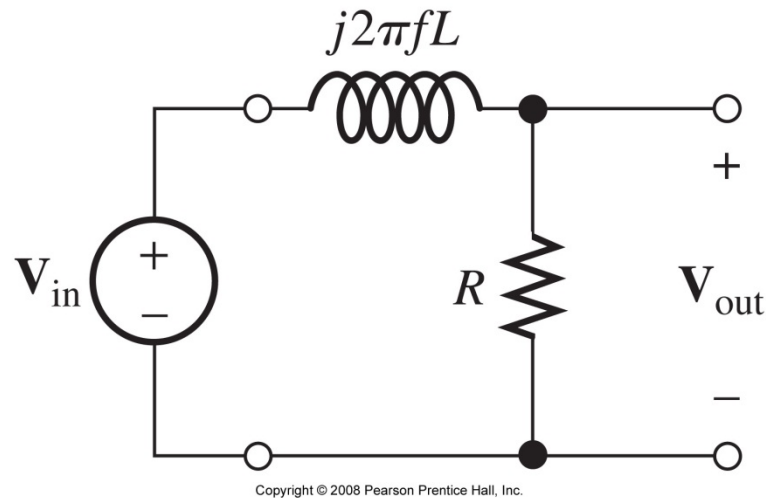


✓ We've seen one way of creating a low pass filter using an RC network

✓ Are there any alternatives to that?

- ✓ In this case we are using the fact that, at low frequencies, the inductor acts as a short-circuit
- ✓ Conversely, at high frequencies, the inductor acts as an open-circuit

High Pass Filters

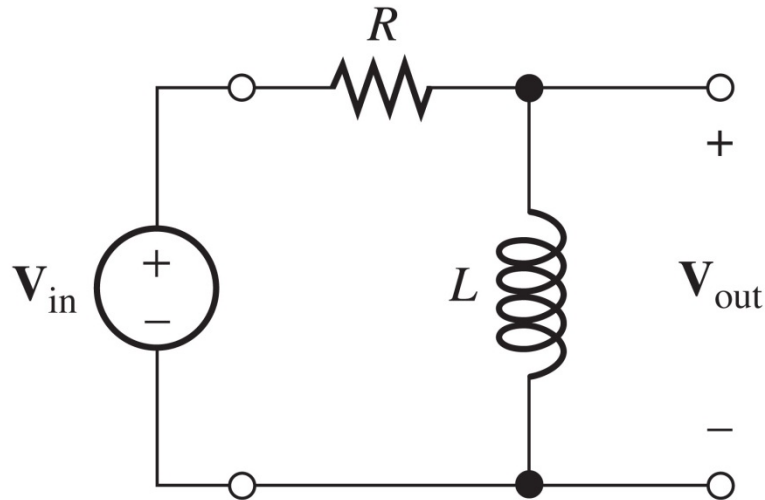
- ✓ We've seen how to create low pass filters using RC and RL networks
- ✓ Any ideas on how we might create a high pass filter?



Copyright © 2008 Pearson Prentice Hall, Inc.

Higher Order Filters

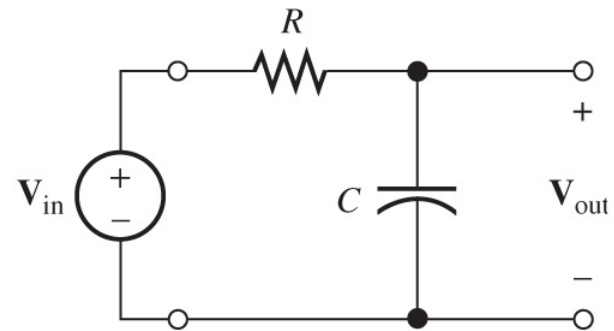
- ✓ As we've seen, we can get a certain amount of rejection per decade or octave with an RC or RL filter
- ✓ Suppose we need a greater amount of rejection per decade or octave – is there a solution?



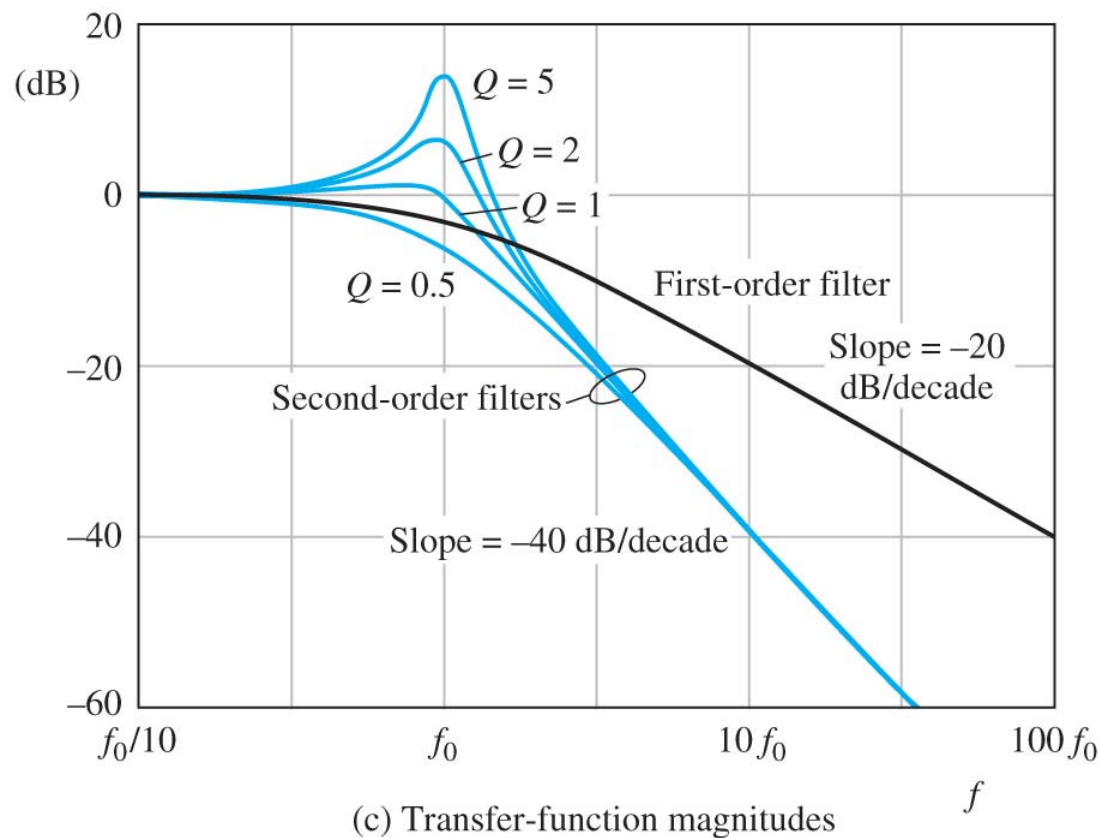(b) First-order lowpass filter

Higher Order Filters

- ✓ A second order filter gives us twice the slope (in dB/decade) as compared to a first order filter




$$|H(f)|_{\text{dB}} = 20 \log |H(f)|$$


$ H(f) $	$ H(f) _{\text{dB}}$
100	40
10	20
2	6
$\sqrt{2}$	3
1	0
$1/\sqrt{2}$	-3
1/2	-6

Band Reject Filters

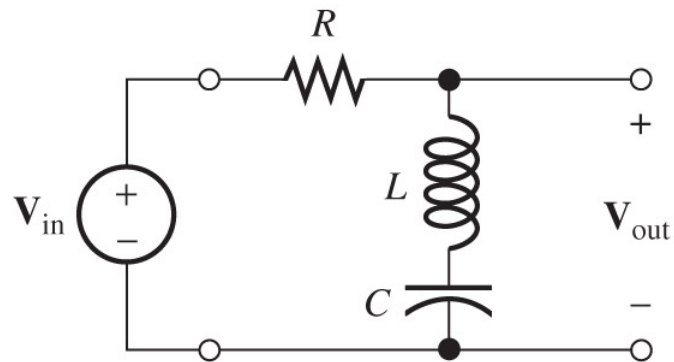
- ✓ Suppose we need a band reject filter – a filter that lets through low and high frequencies, but doesn't let through any frequencies in the middle
- ✓ How might we build such a filter?



Band Reject Filters

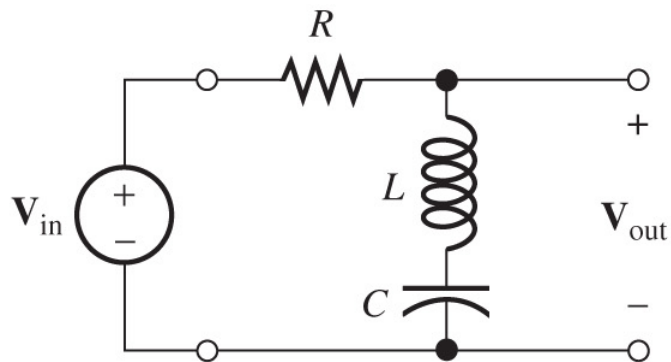


(a) Circuit diagram

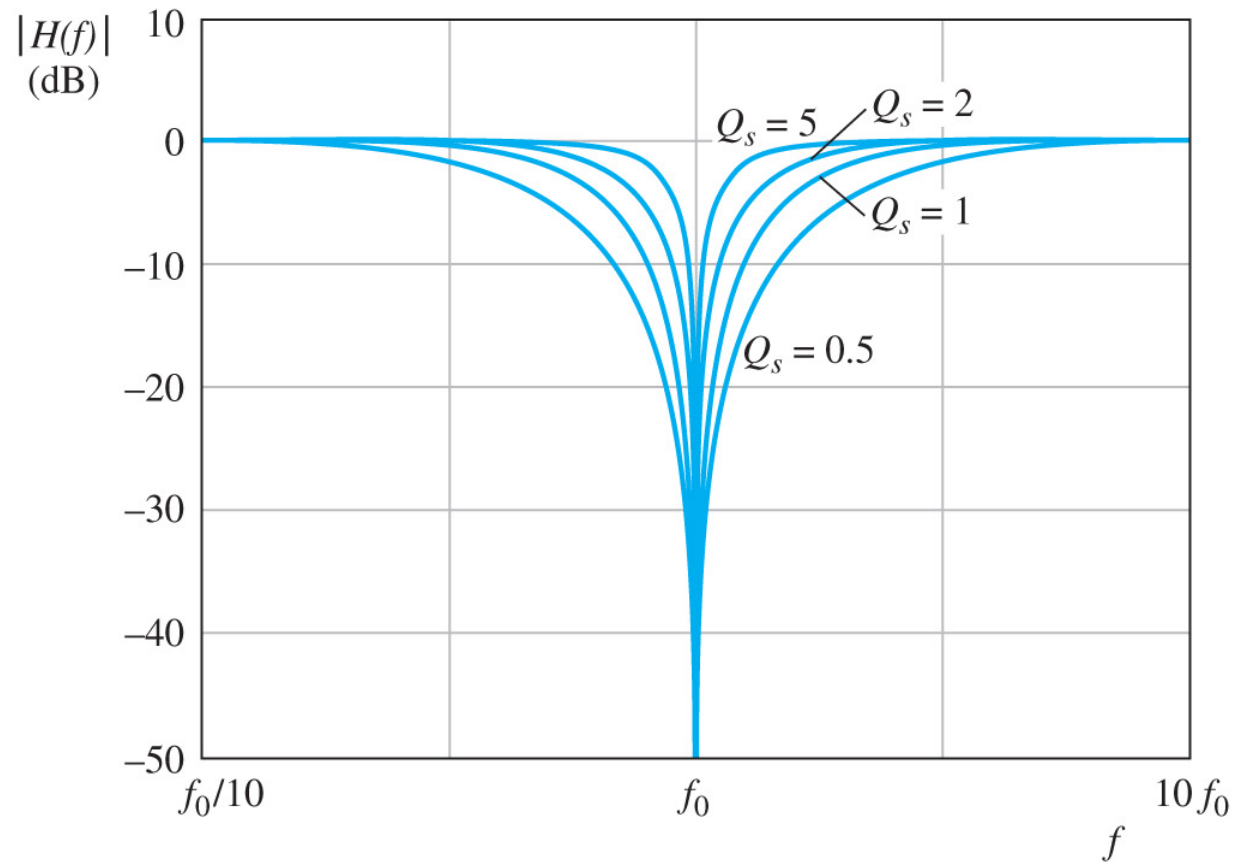


(b) Transfer-function magnitude

Band Pass Filter

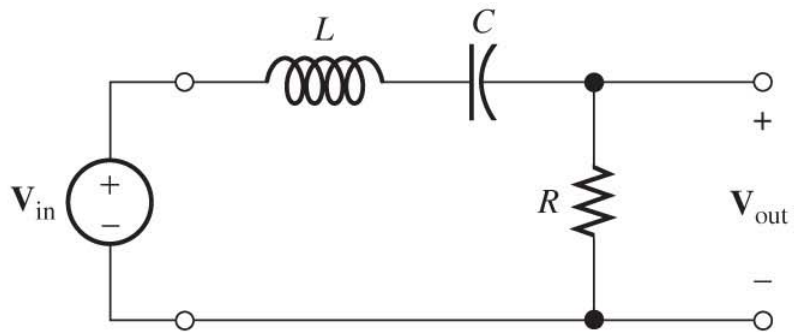

(a) Circuit diagram

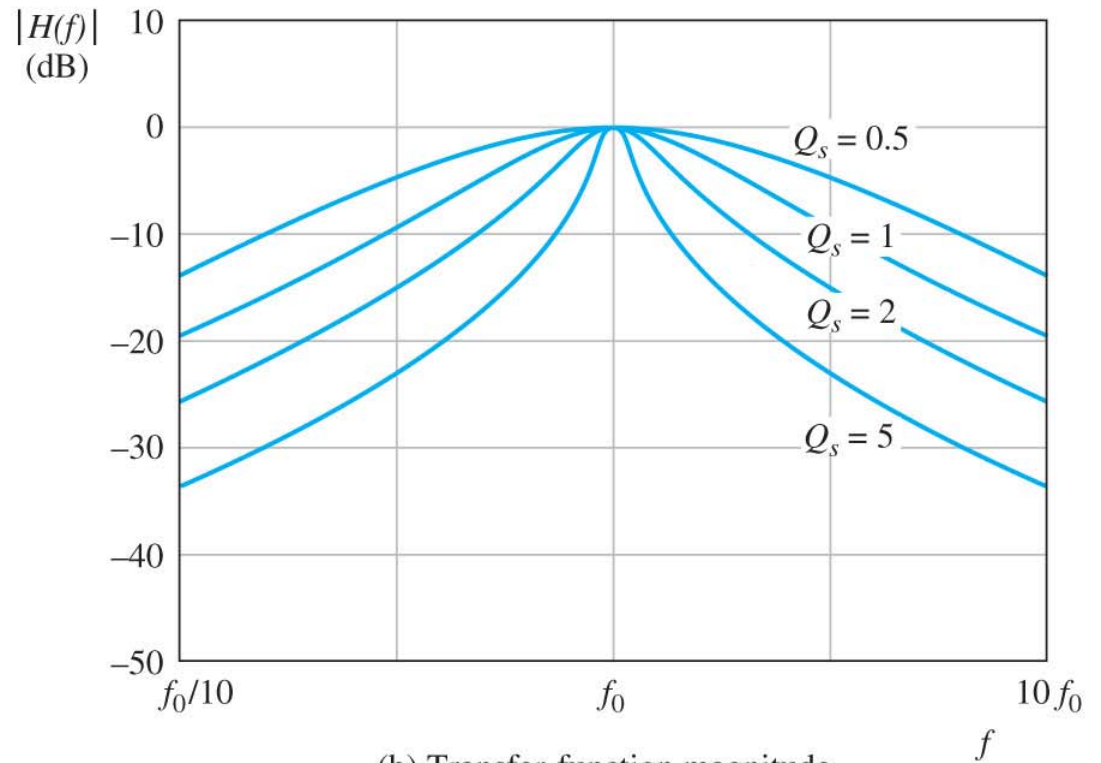


(b) Transfer-function magnitude

Quality Factor


- ✓ What are the Q values all about?
- ✓ These reflect the Quality Factor for the circuit
- ✓ What is the impedance Z_s in the circuit below?

$$Z_s = R + j2\pi fL - j\frac{1}{2\pi fC}$$

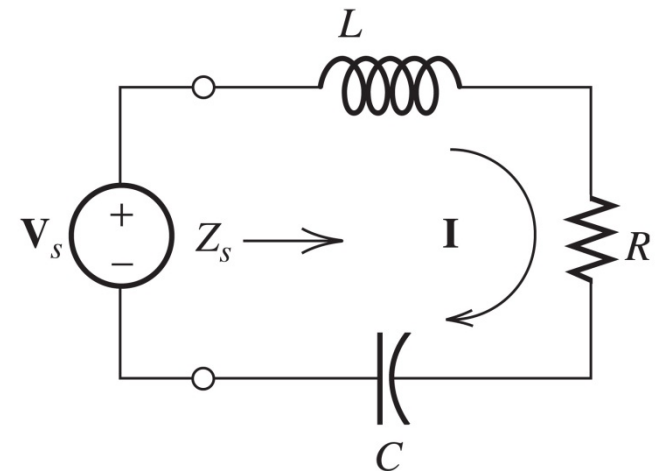- ✓ There will be a frequency f_0 where, for particular values of L and C , the two imaginary components cancel each other out



Quality Factor

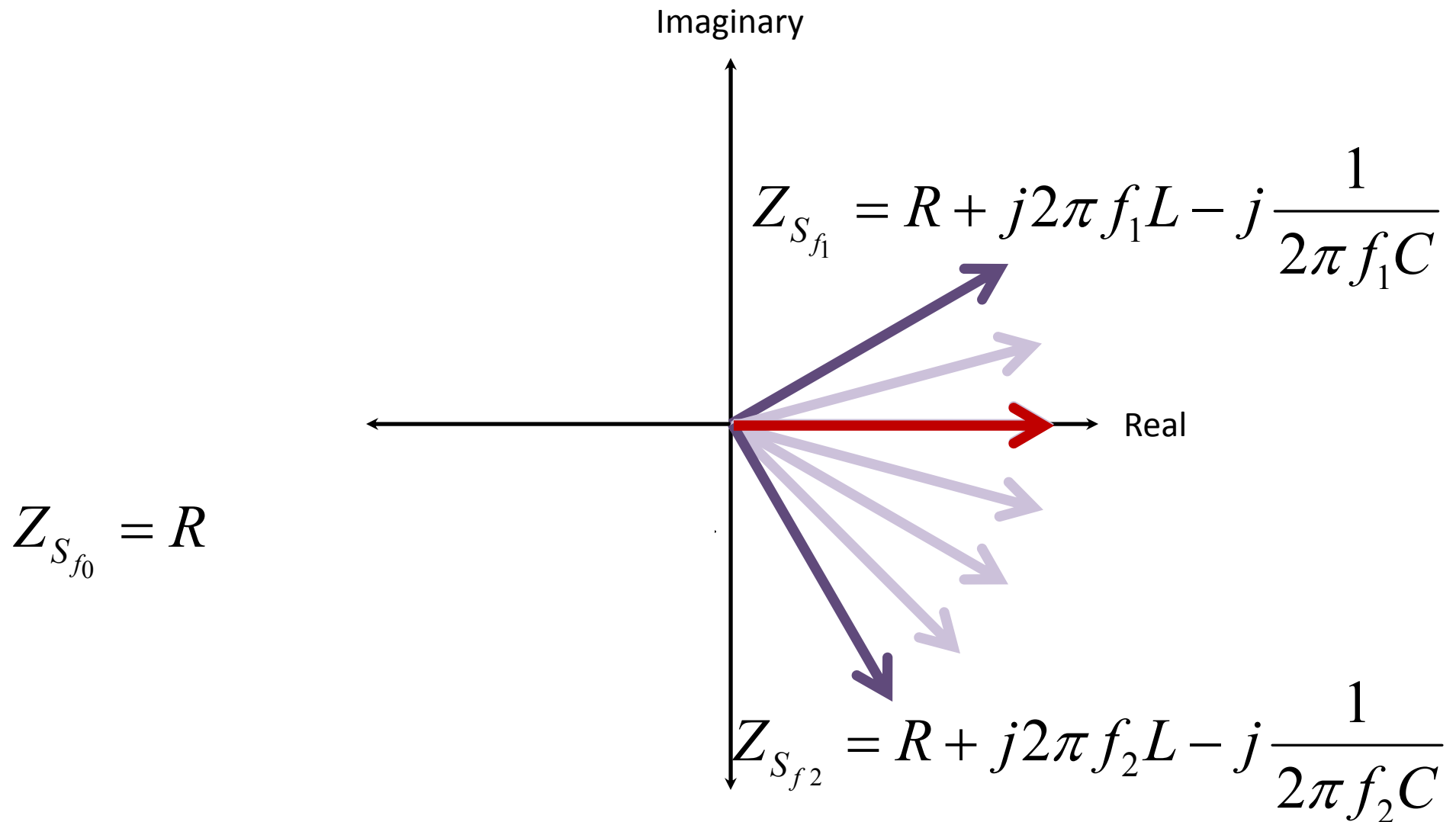

Quality Factor


✓ That frequency will be when the following is true:

$$2\pi f_o L = \frac{1}{2\pi f_o C}$$

✓ Solving for f_0 we get:

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

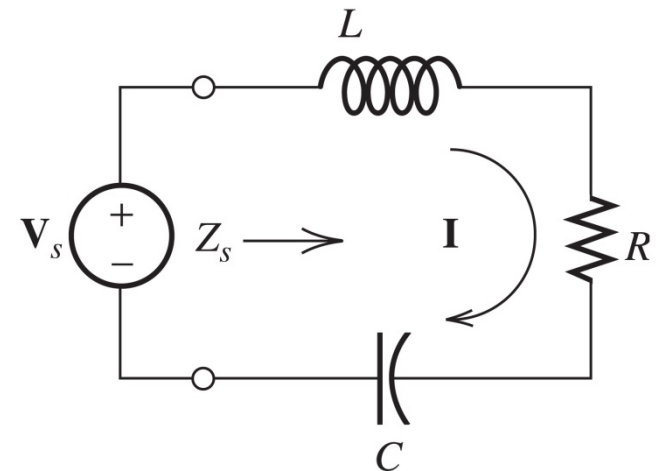✓ This is called the resonant frequency of the circuit




Quality Factor

- ✓ The Quality Factor for this (series) circuit is defined as:

$$Q_s = \frac{2\pi f_0 L}{R}$$


- ✓ Substituting in the previously derived equation for the resonant frequency f_0 and solving for L we can also get:

$$Q_s = \frac{1}{2\pi f_0 CR}$$

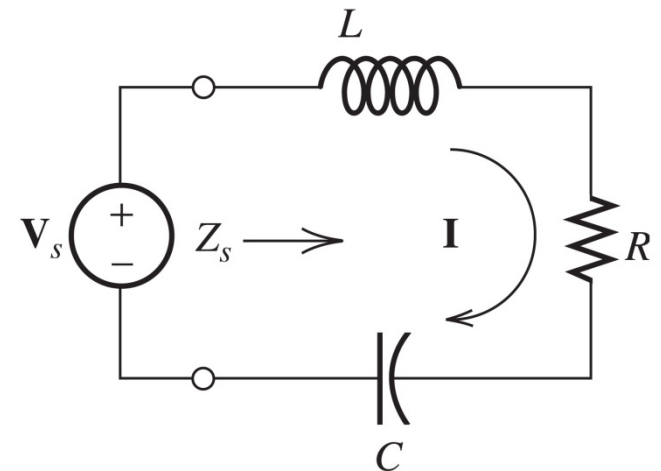


Quality Factor

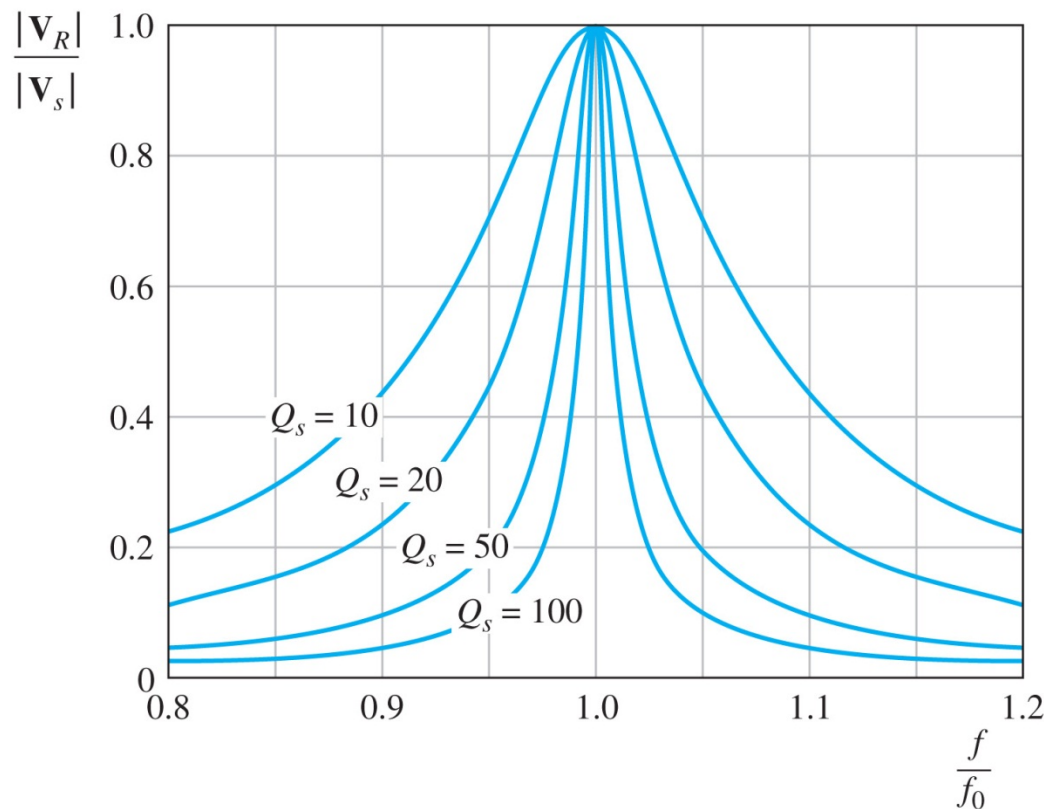- ✓ For our series resonant band pass filter we can see how things change as we vary the value of Q_s





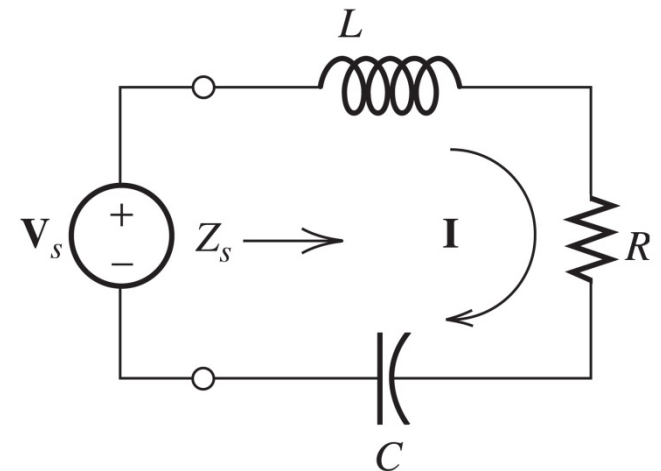Copyright © 2008 Pearson Prentice Hall, Inc.



Bandwidth

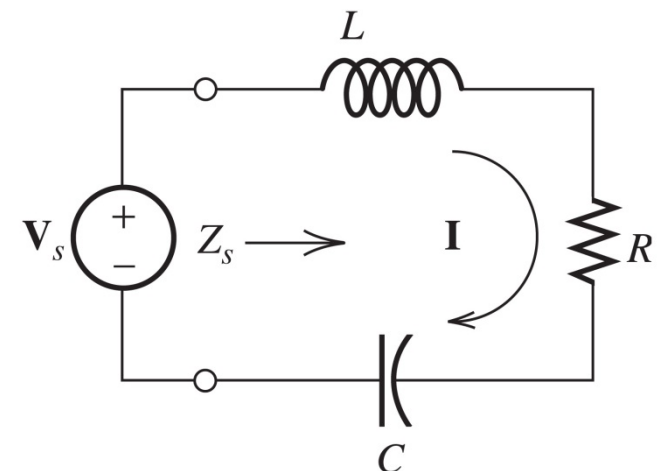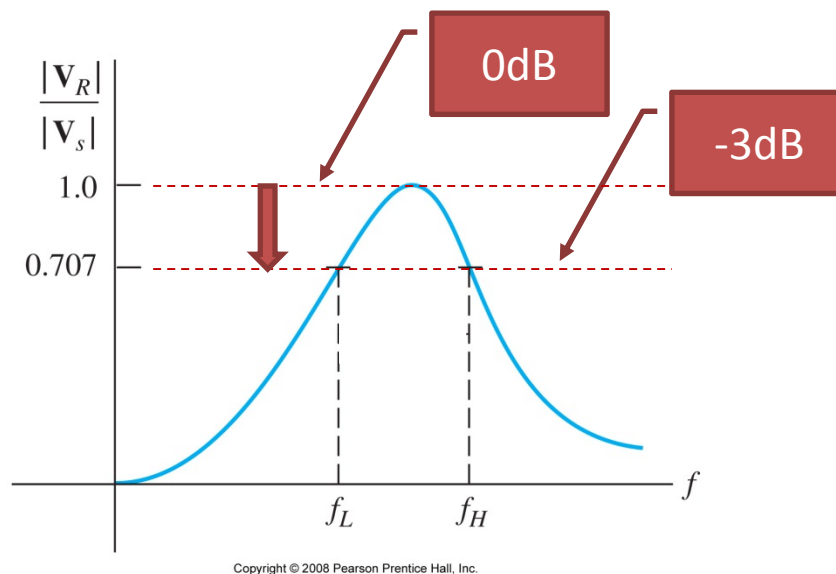- ✓ For a given Q_S , let's look at the half-power frequencies
- ✓ Recall this is where the value of the transfer function is at 0.707
- ✓ Call these frequencies f_L and f_H




Bandwidth

- ✓ The bandwidth of the filter is defined as:


$$B = f_H - f_L$$

- ✓ For the series resonant circuit, it can be shown that:

$$B = \frac{f_0}{Q_S}$$

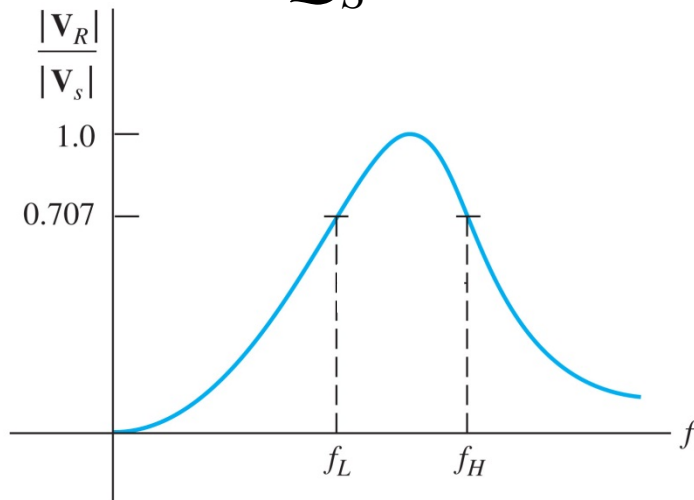

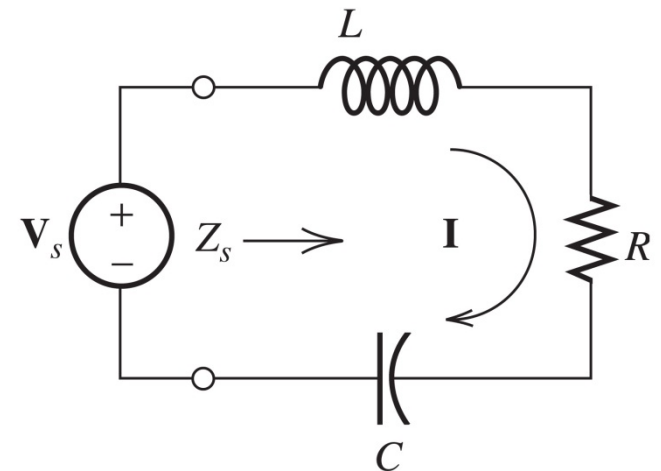
Copyright © 2008 Pearson Prentice Hall, Inc.




Bandwidth

- ✓ Furthermore, for $Q_S \gg 1$, the half-power frequencies are given by:
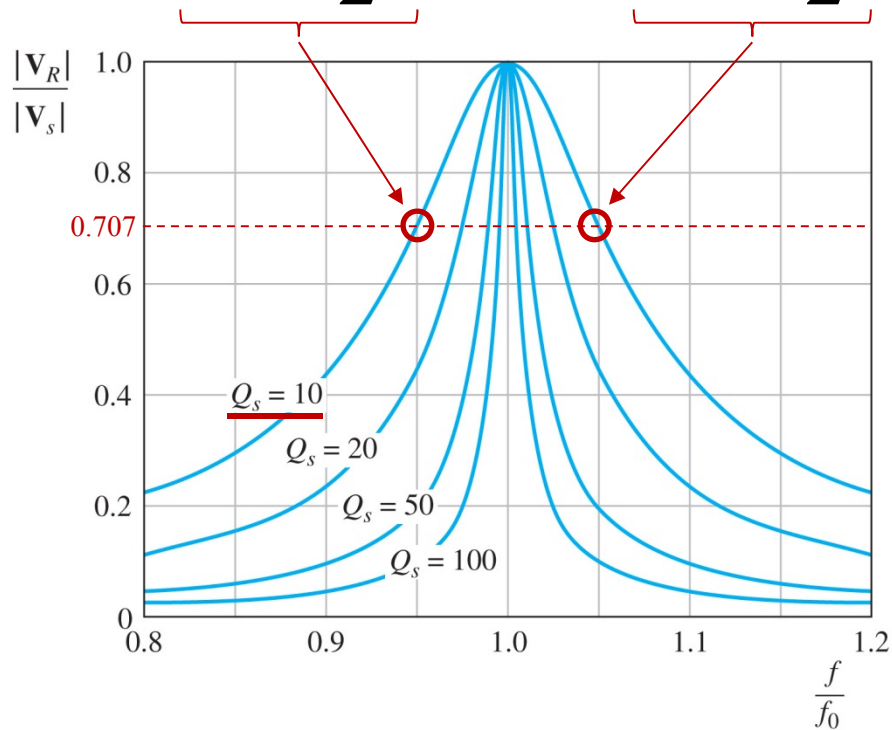
$$f_L \cong f_0 - \frac{B}{2}; \quad f_H \cong f_0 + \frac{B}{2}$$



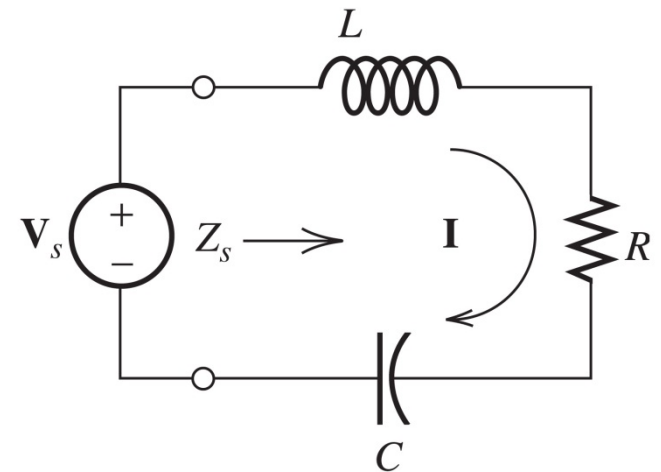
Copyright © 2008 Pearson Prentice Hall, Inc.



Bandwidth

- ✓ Furthermore, for $Q_S \gg 1$, the half-power frequencies are given by:
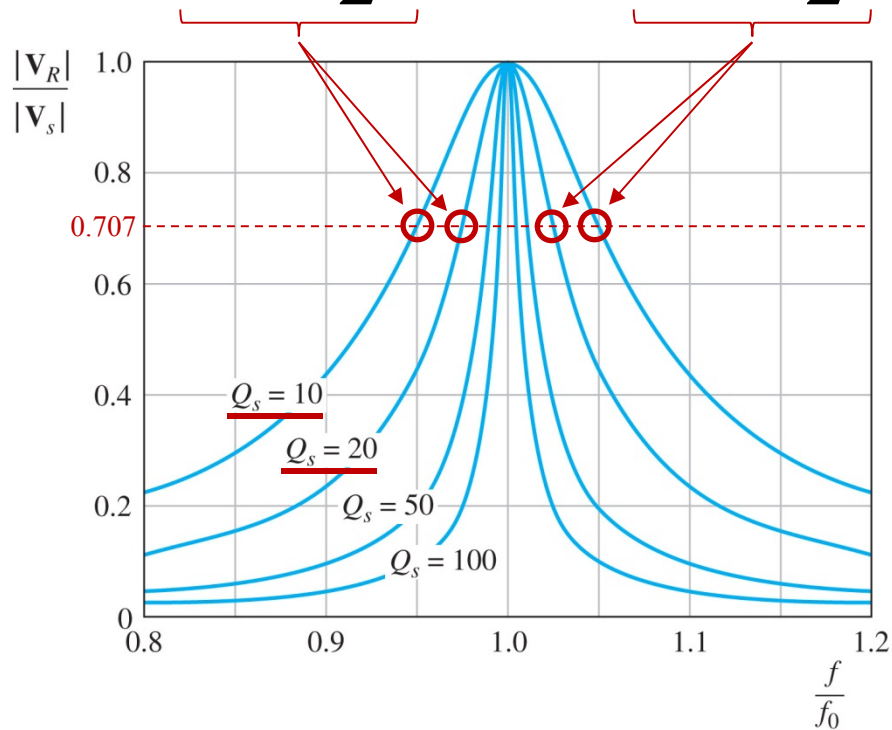
$$f_L \cong f_0 - \frac{B}{2}; \quad f_H \cong f_0 + \frac{B}{2}$$



Copyright © 2008 Pearson Prentice Hall, Inc.

